

Week6

2학년 2반 2021041089 최태민

유튜브 영상 주소

실습 1 : <https://youtu.be/2qOY2NzABxk>

실습 2 : <https://youtu.be/-r-CvaiYMWE>

과제 1 : <https://youtu.be/sDVg5UrgNhM>


과제 2 : <https://youtu.be/YLviLQWIdIU>

실습 1 : 동작표


입력 출력 동작 Table								
X1 (스위치)	X2 (스위치)		Y2	Y3	Y4	Y5	Y6	Y7
0	0		1	0	1	0	1	0
0	1		1	0	0	1	0	1
1	0		1	0	0	1	0	1
1	1		0	1	0	1	1	0

입력 출력 동작 Table		
입력 스위치 X0	출력 LED Y0	출력 LED Y1
0	1	0
1	0	1

실습 1 : 가상회로, fpga 회로

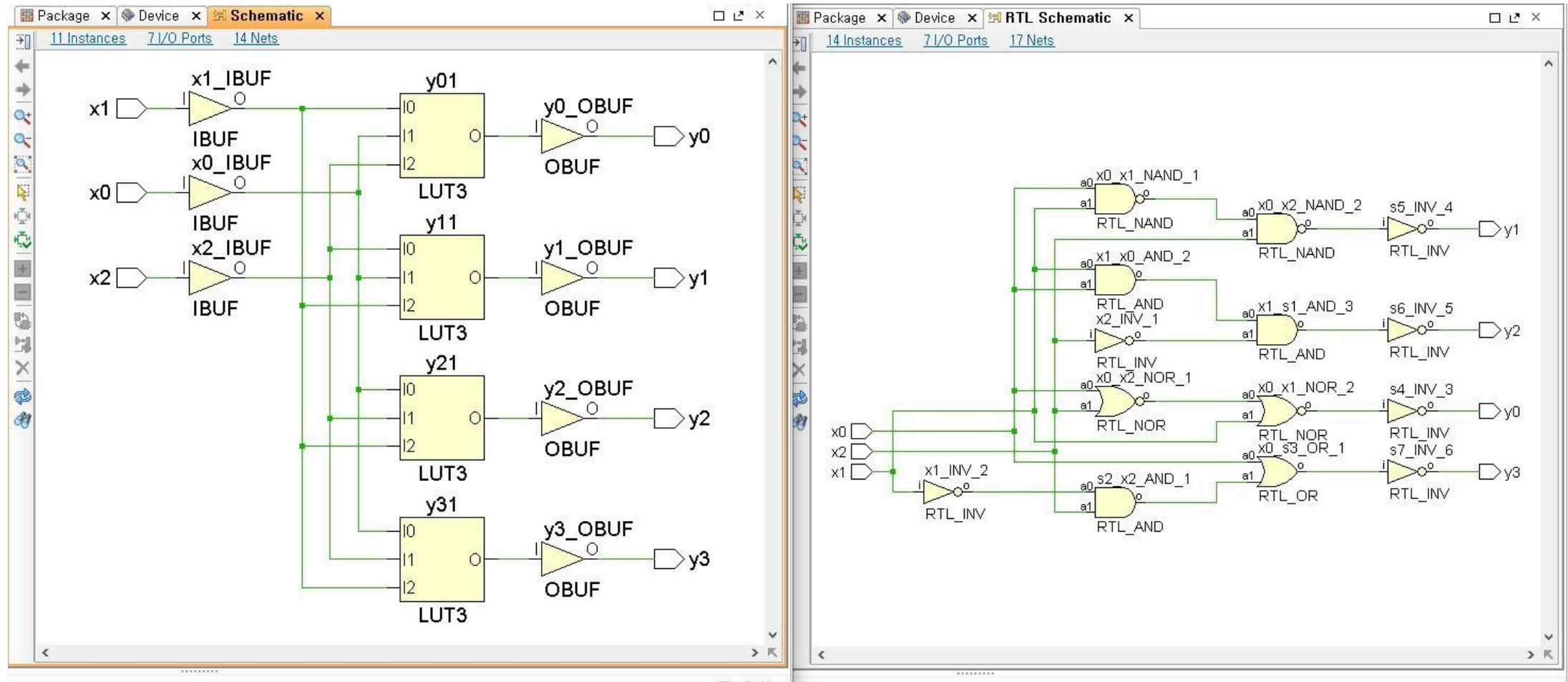



실습 1 : 시뮬레이션 화면

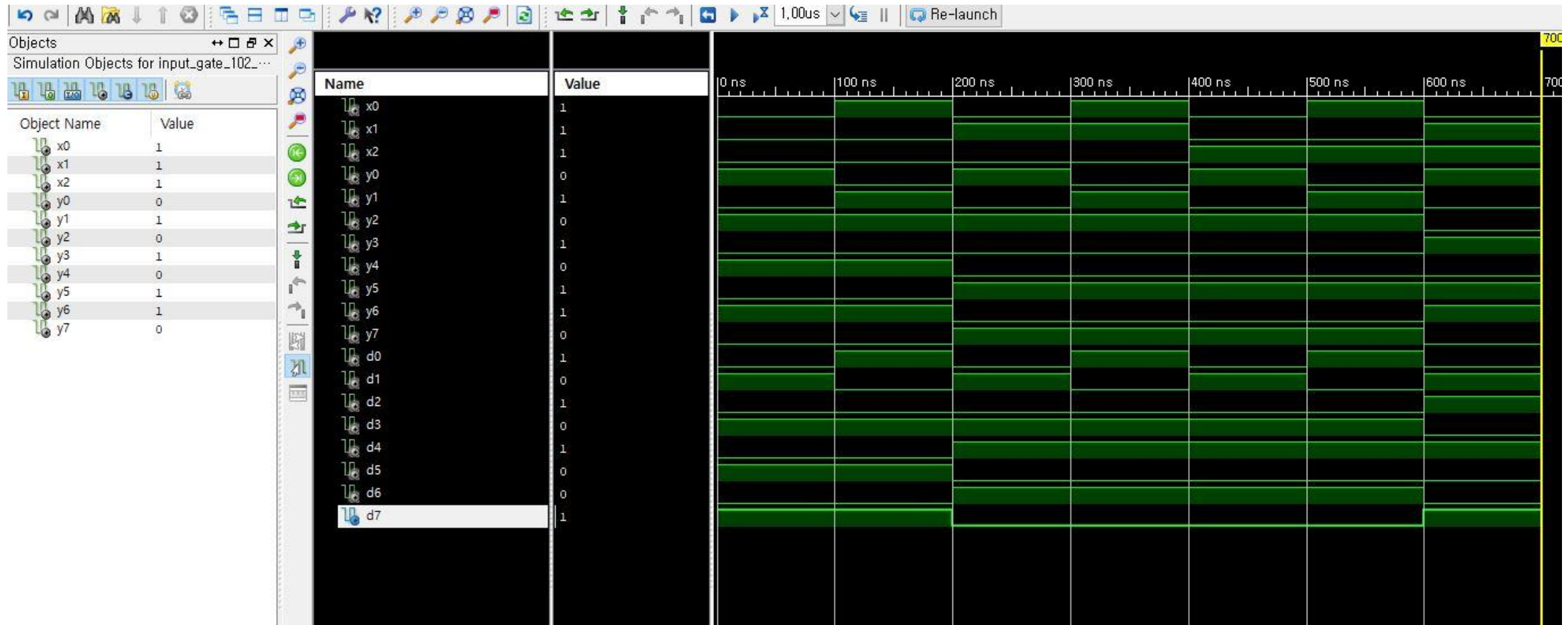


실습 2 : 동작표

input			output			
x2	x1	x0	y0	y1	y2	y3
0	0	0	1	0	1	1
0	0	1	0	0	1	0
0	1	0	1	0	1	1
0	1	1	1	0	0	0
1	0	0	0	1	1	0
1	0	1	0	1	1	0
1	1	0	1	1	1	1
1	1	1	1	0	1	0

실습 2 : 가상회로, fpga 회로

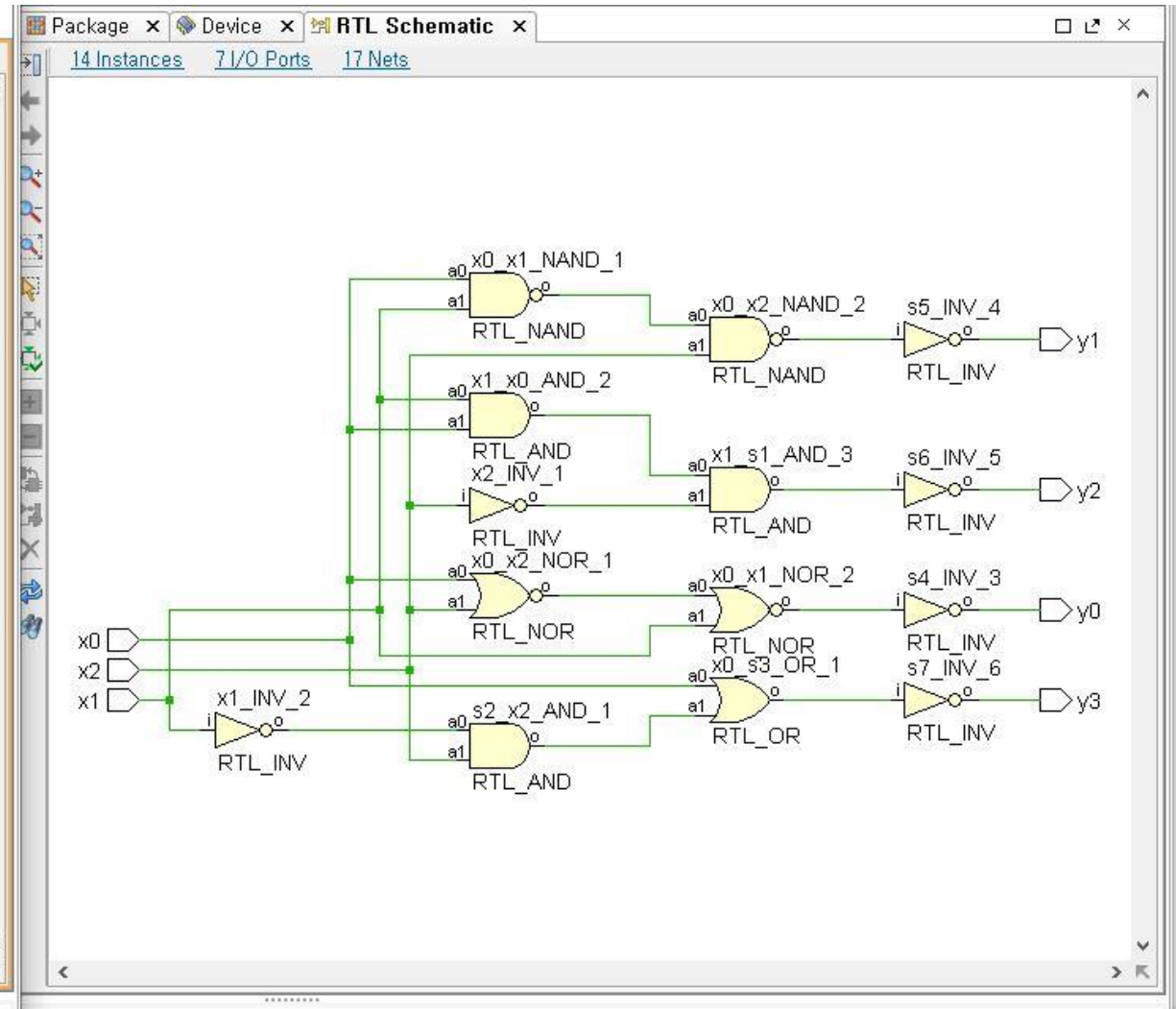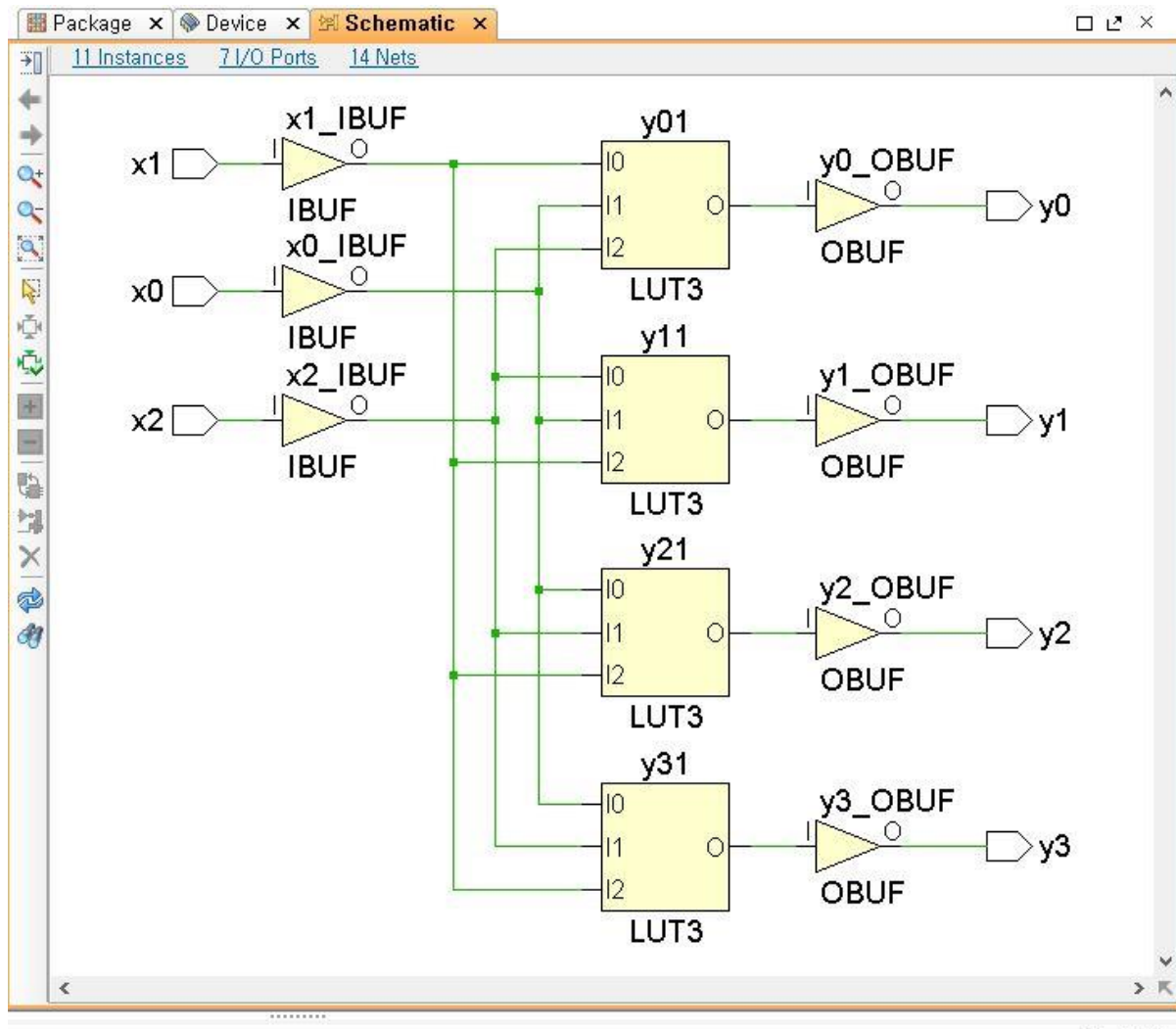


실습 2 : 시뮬레이션 화면

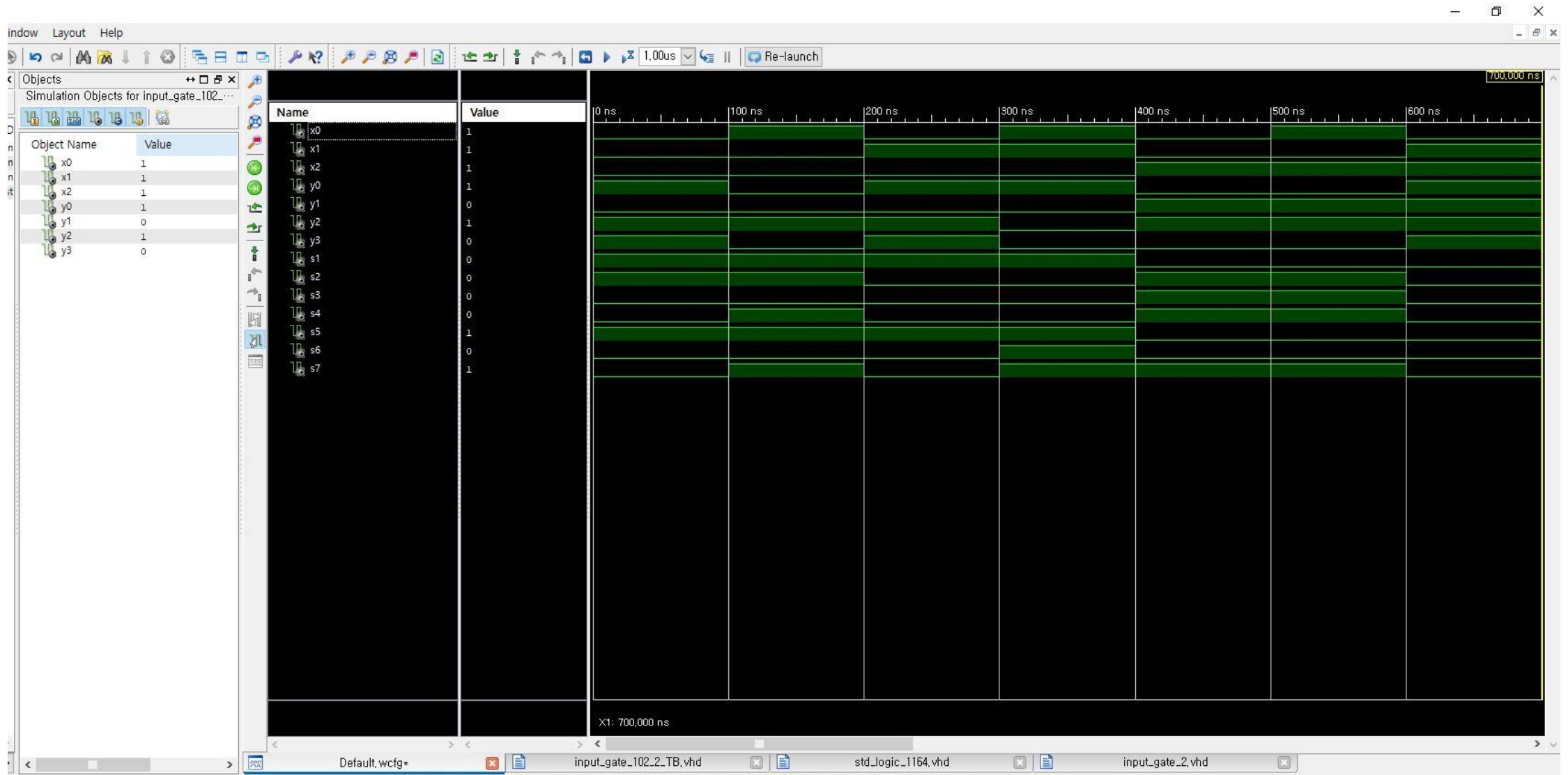


과제 1 : 동작표

input			output
x2	x1	x0	y0
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

과제 1 : 가상회로, fpga 회로

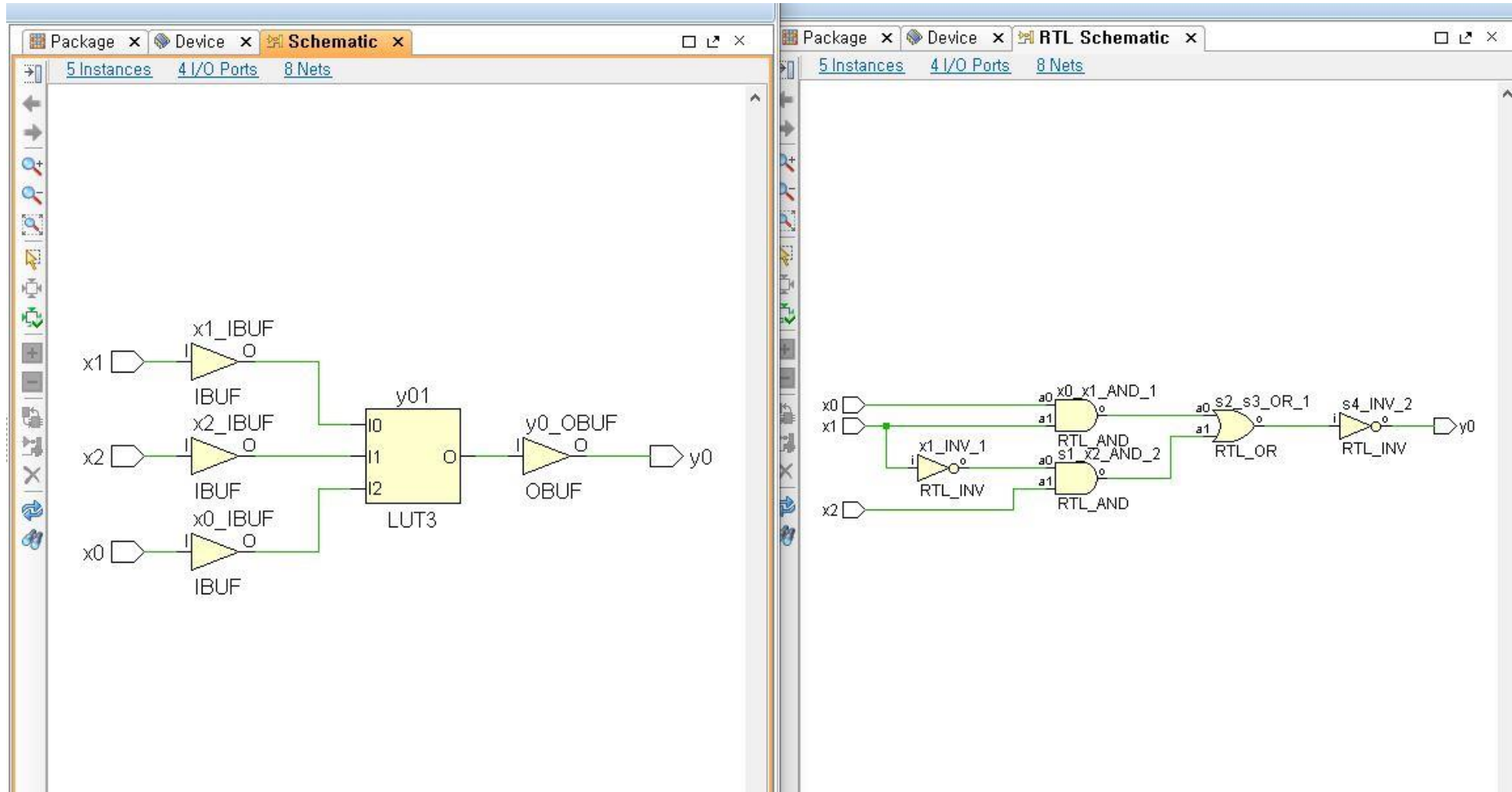


과제 1 : 시뮬레이션 화면

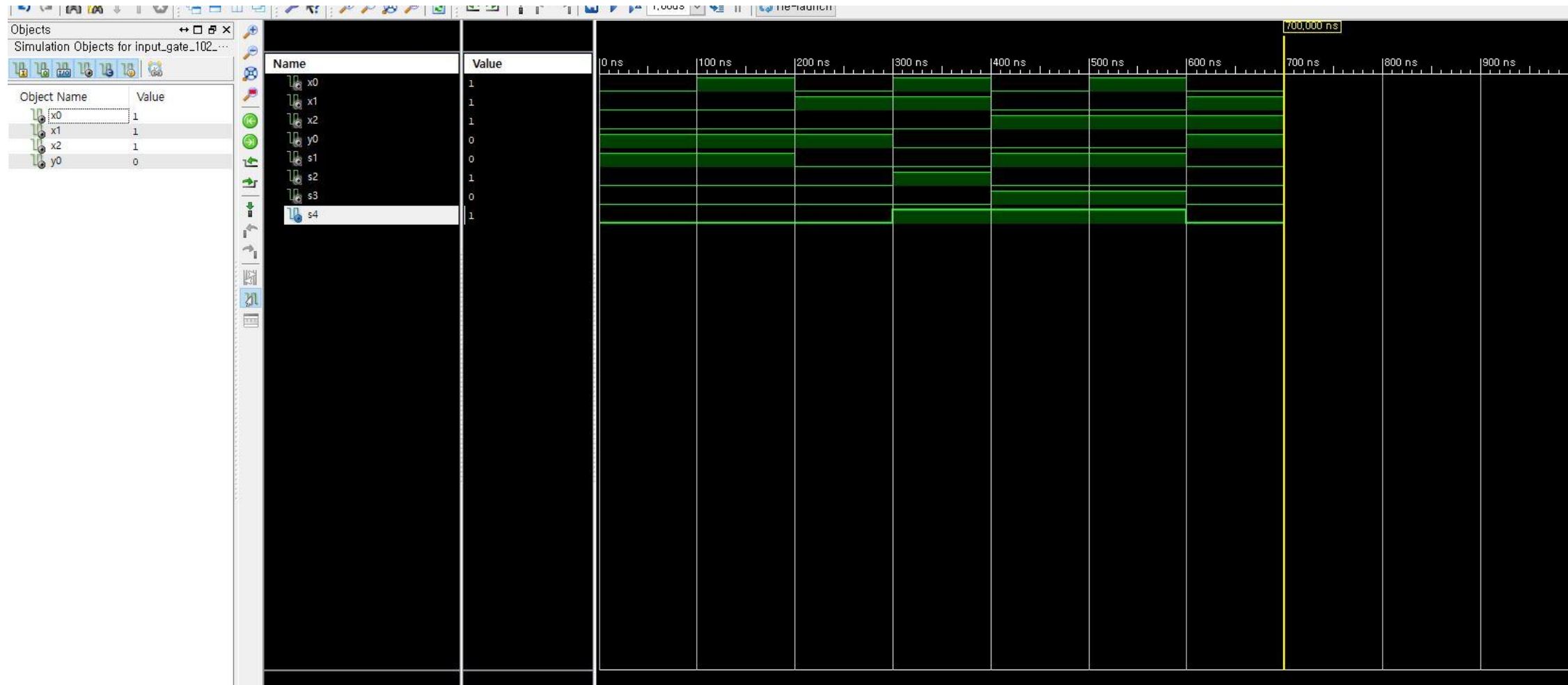

과제 2 : 동작표

input				output			
x0	x1	x2	x3	y0	y1	y2	y3
0	0	0	0	0	0	1	1
1	0	0	0	0	1	0	0
0	1	0	0	0	1	0	0
1	1	0	0	1	0	1	1
0	0	1	0	0	1	1	1
1	0	1	0	0	0	0	0
1	1	1	0	0	0	0	0
0	0	0	1	1	1	1	1
1	0	0	1	0	0	1	1
0	1	0	1	0	1	0	0
1	1	0	1	0	1	0	0
0	0	1	1	1	0	1	1
1	0	1	1	1	1	1	1
1	1	1	1	1	0	0	0

과제 2 : 가상회로, fpga 회로

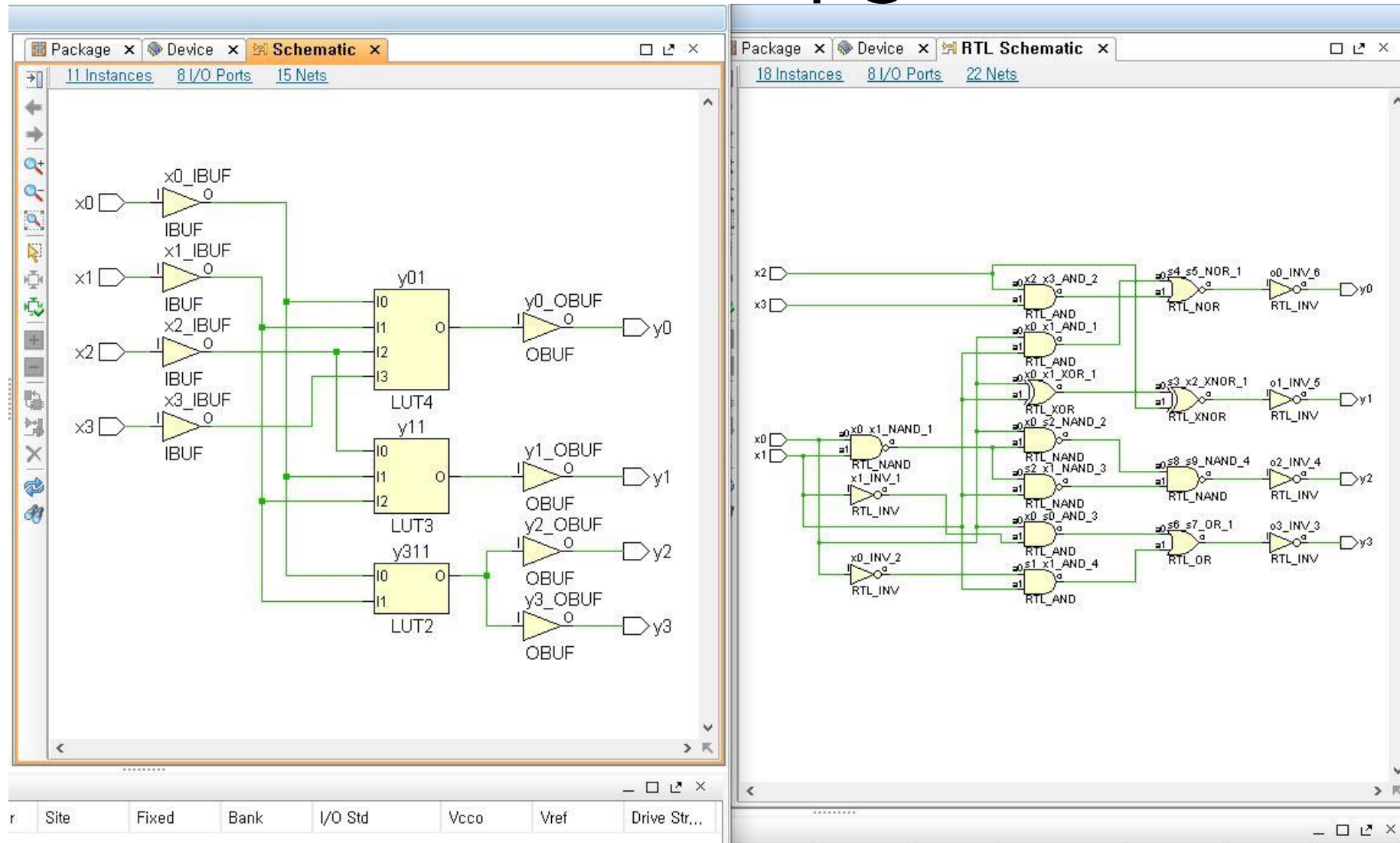

과제 2 : 시뮬레이션 화면

