

week5



2학년_2반_2021041089_최태민

유튜브 영상 주소 : <https://www.youtube.com/watch?v=l2-7cLv8yA>

과제 : 동작테이블

A (입력)	B (입력)	C (입력)	Y0 (3입력AND) (A x B) C = Y0	Y1 (3입력OR) (A + B) + C = Y0	Y2 (3입력XOR) (A ⊕ B) ⊕ C = Y1	Y3 (1입력A) (invertor) $\overline{A} = Y4$	Y4 (1입력A) (Buffer) A = Y4
0	0	0	0	0	0	1	0
1	0	0	0	1	1	0	1
0	1	0	0	1	1		
0	0	1	0	1	1		
1	1	0	0	1	0		
0	1	1	0	1	0		
1	0	1	0	1	0		
1	1	1	1	1	1		

과제 : 가상회로, FPGA 회로

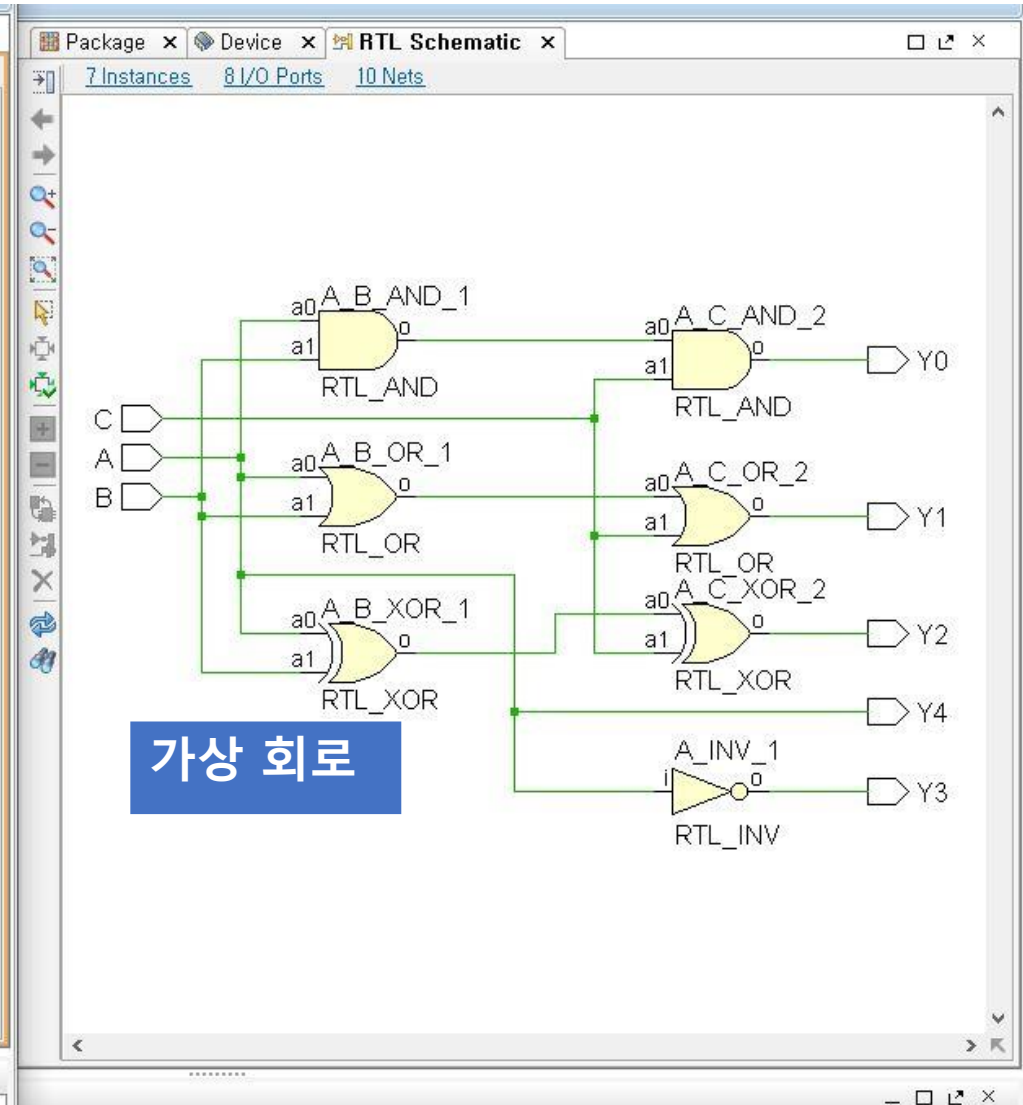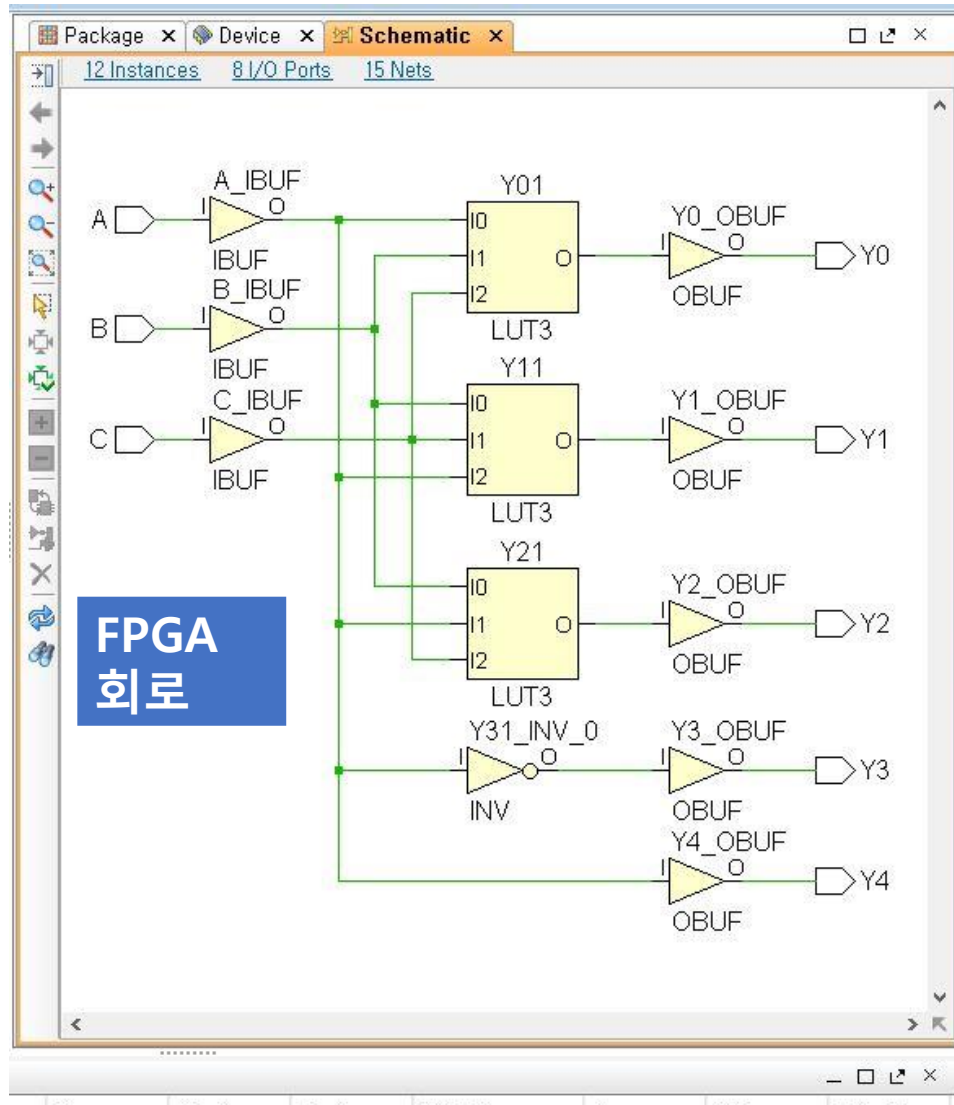

과제 : 시뮬레이션 화면

