


week4

2학년 2반 2021041089_최태민


실습1 입력, 출력 (동작테이블)

입력 출력 동작 Table	
입력 스위치 X7	출력 LED Y7
0	0
1	1

실습1 입력, 출력 (가상회로, fpga 회로)

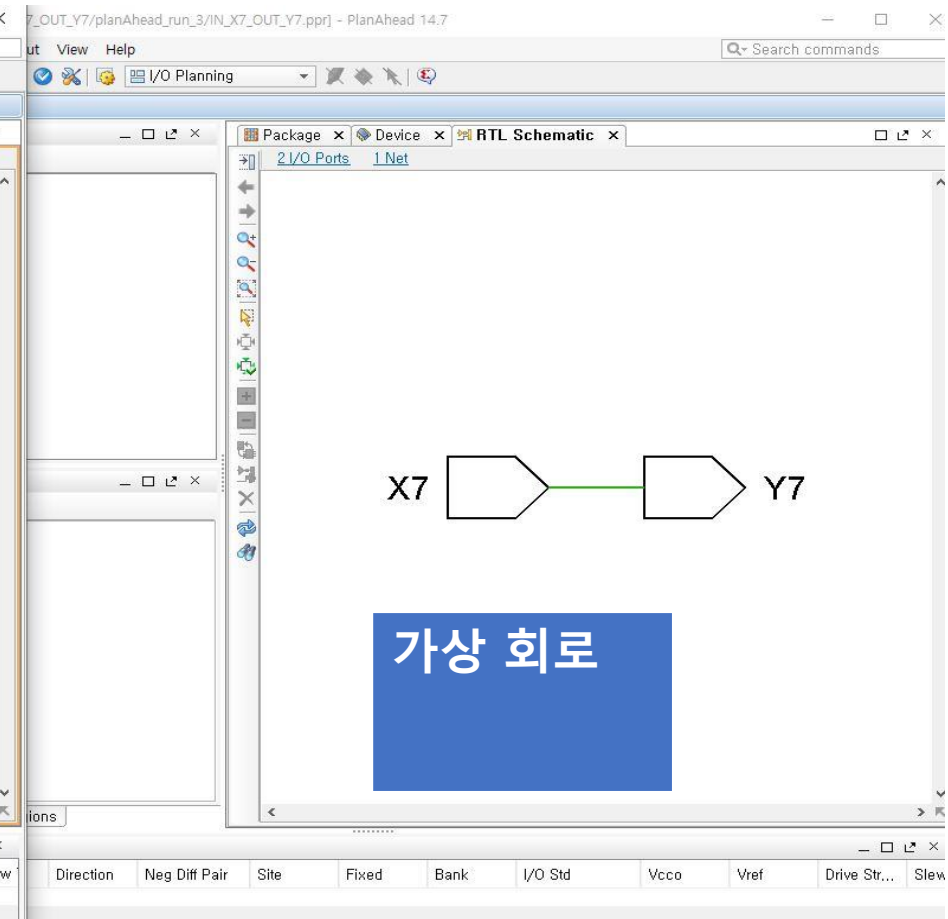


실습1 입력, 출력 (시뮬레이션 화면)

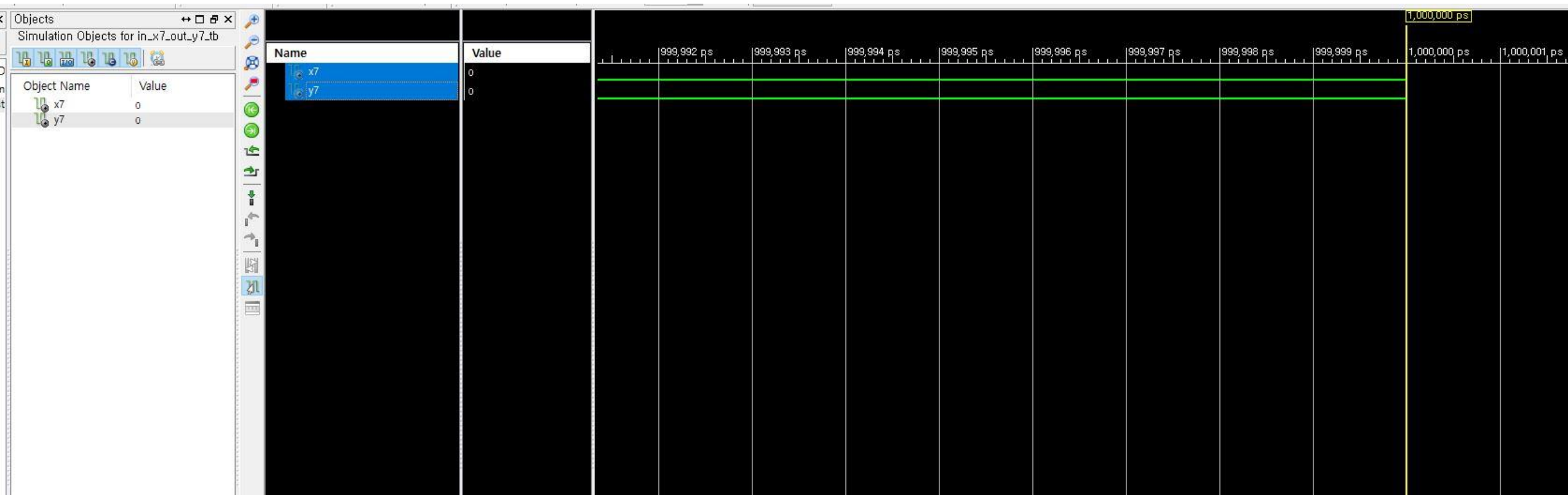


실습2 AND게이트 (동작테이블)

입력 출력 동작 Table		
X0 (스위치)	X1 (스위치)	Y0 (LED)
0	0	0
0	1	0
1	0	0
1	1	1

실습2 AND게이트 (가상회로, fpga 회로)

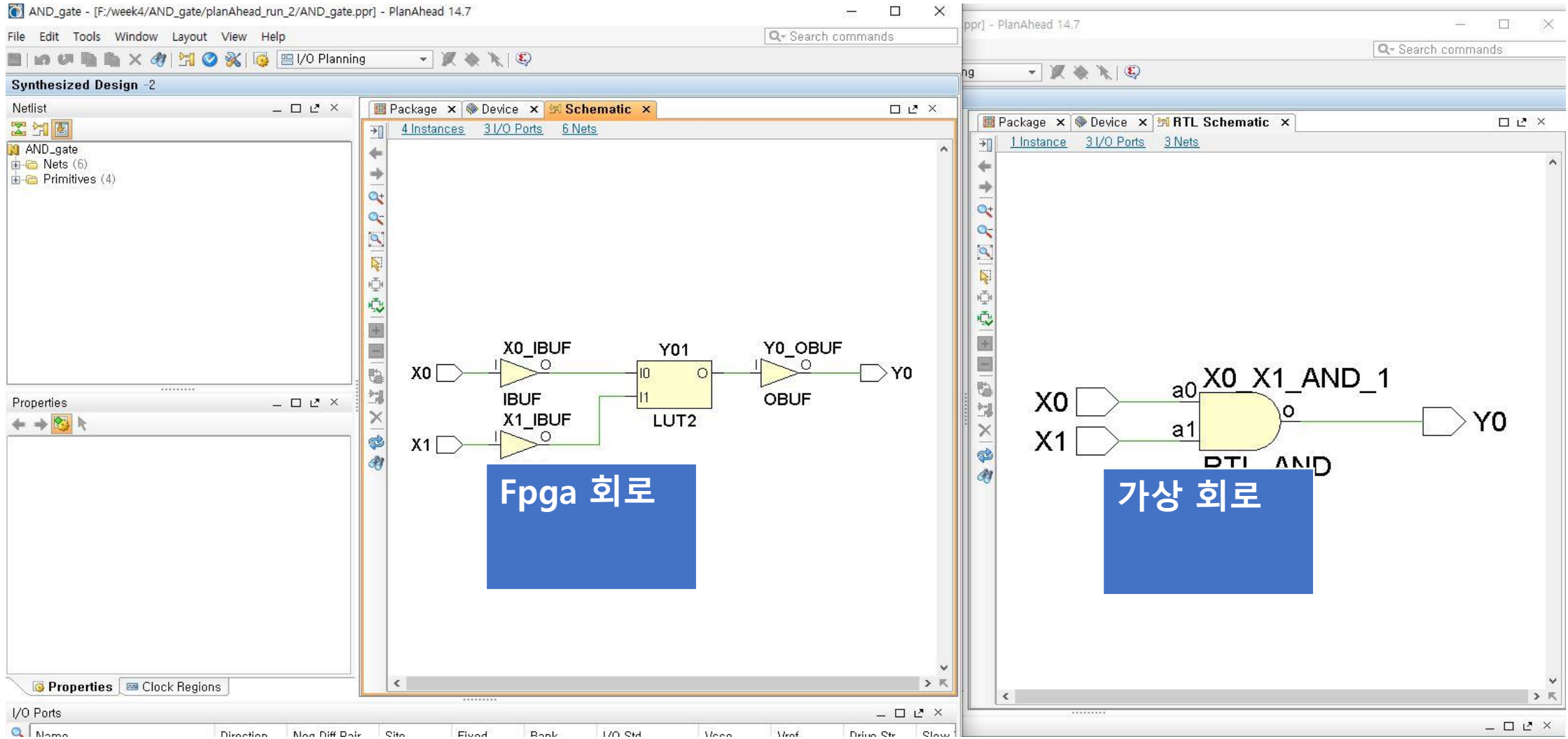



실습2 AND게이트 (시뮬레이션 화면)

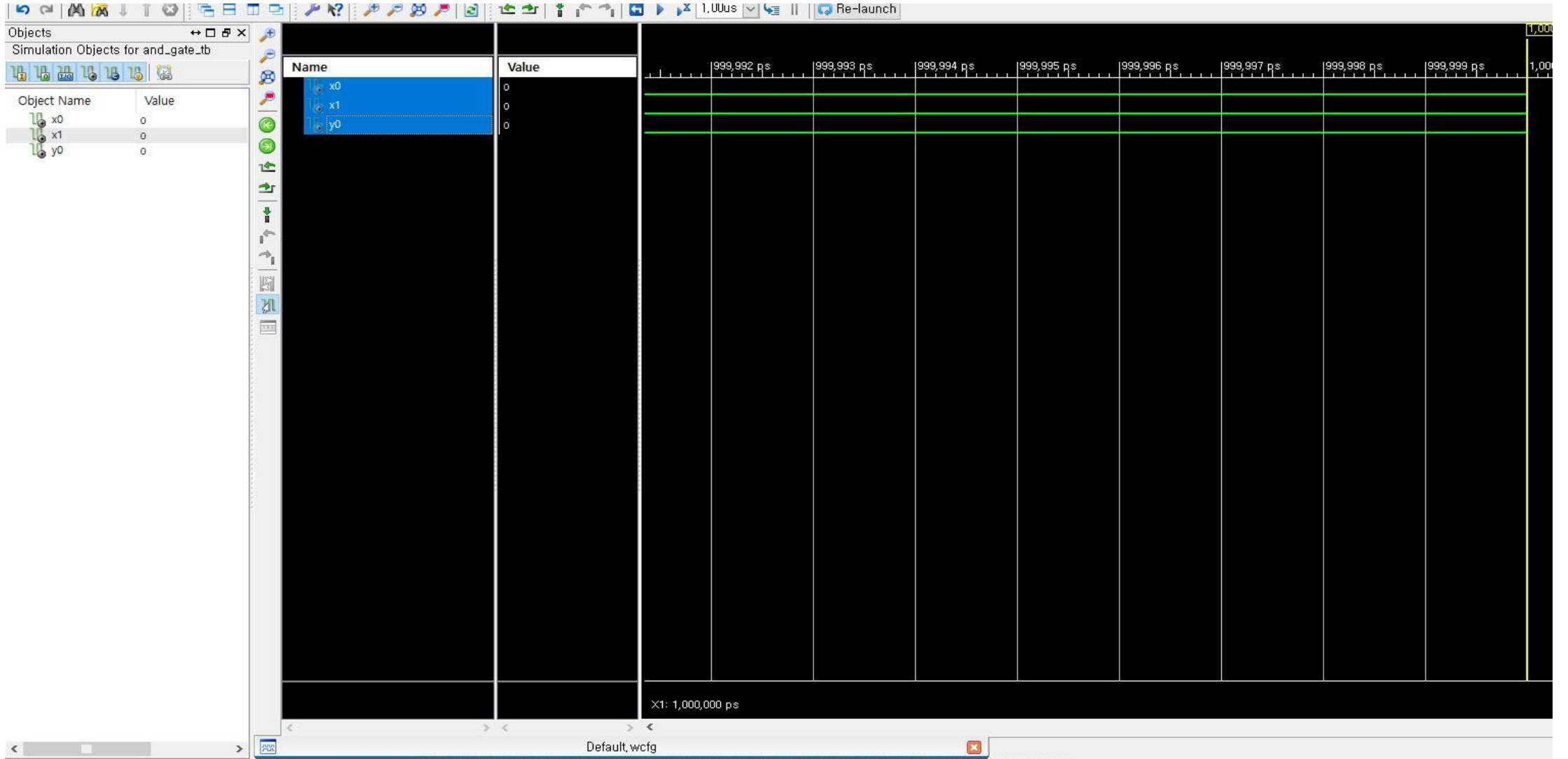


실습3 OR게이트 (동작테이블)

입력 출력 동작 Table			
X0 (스위치)	X1 (스위치)	X2 (스위치)	Y0 (LED)
0	0	0	0
1	0	0	1
0	1	0	1
0	0	1	1
1	1	0	1
0	1	1	1
1	0	1	1
1	1	1	1

실습3 OR게이트 (가상회로, fpga 회로)

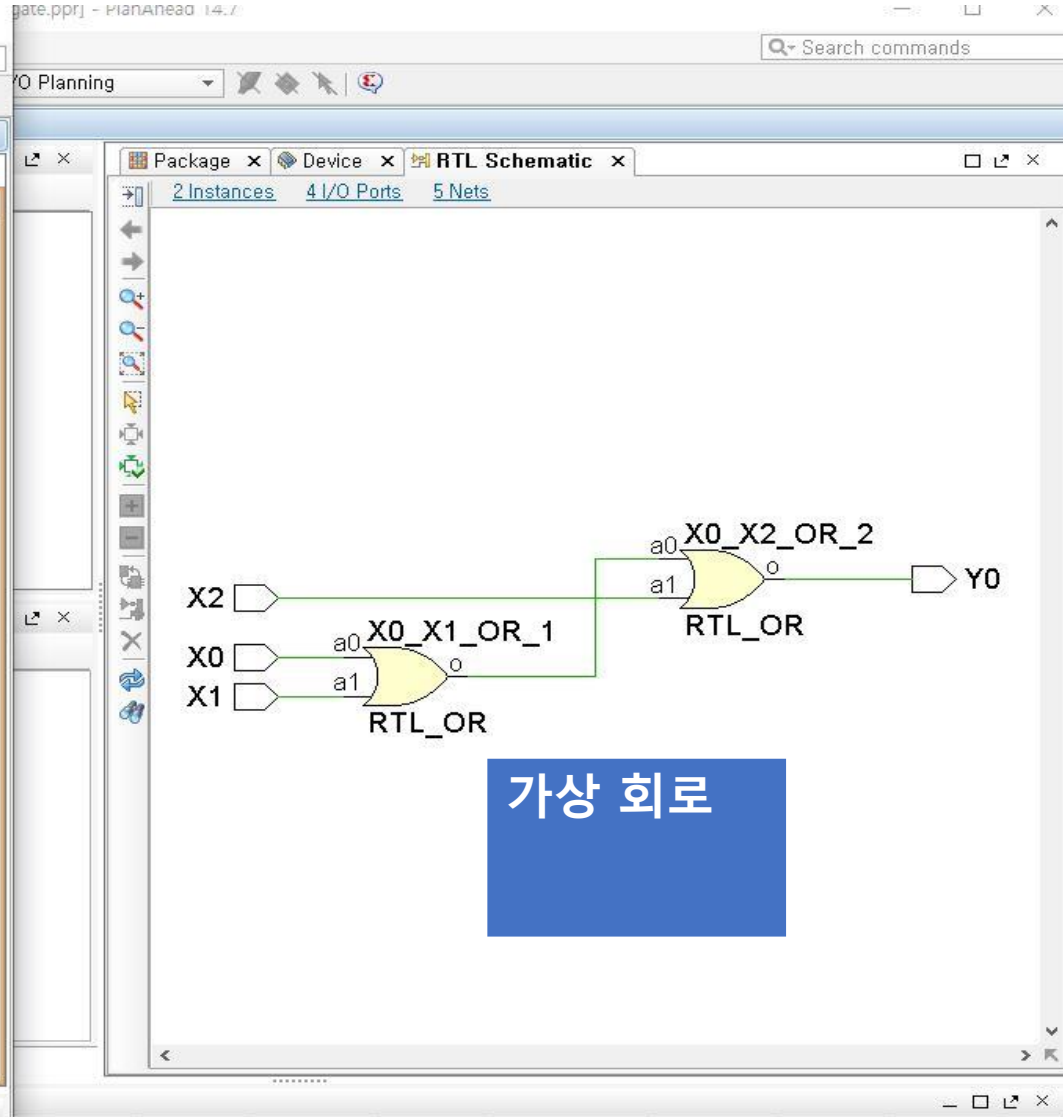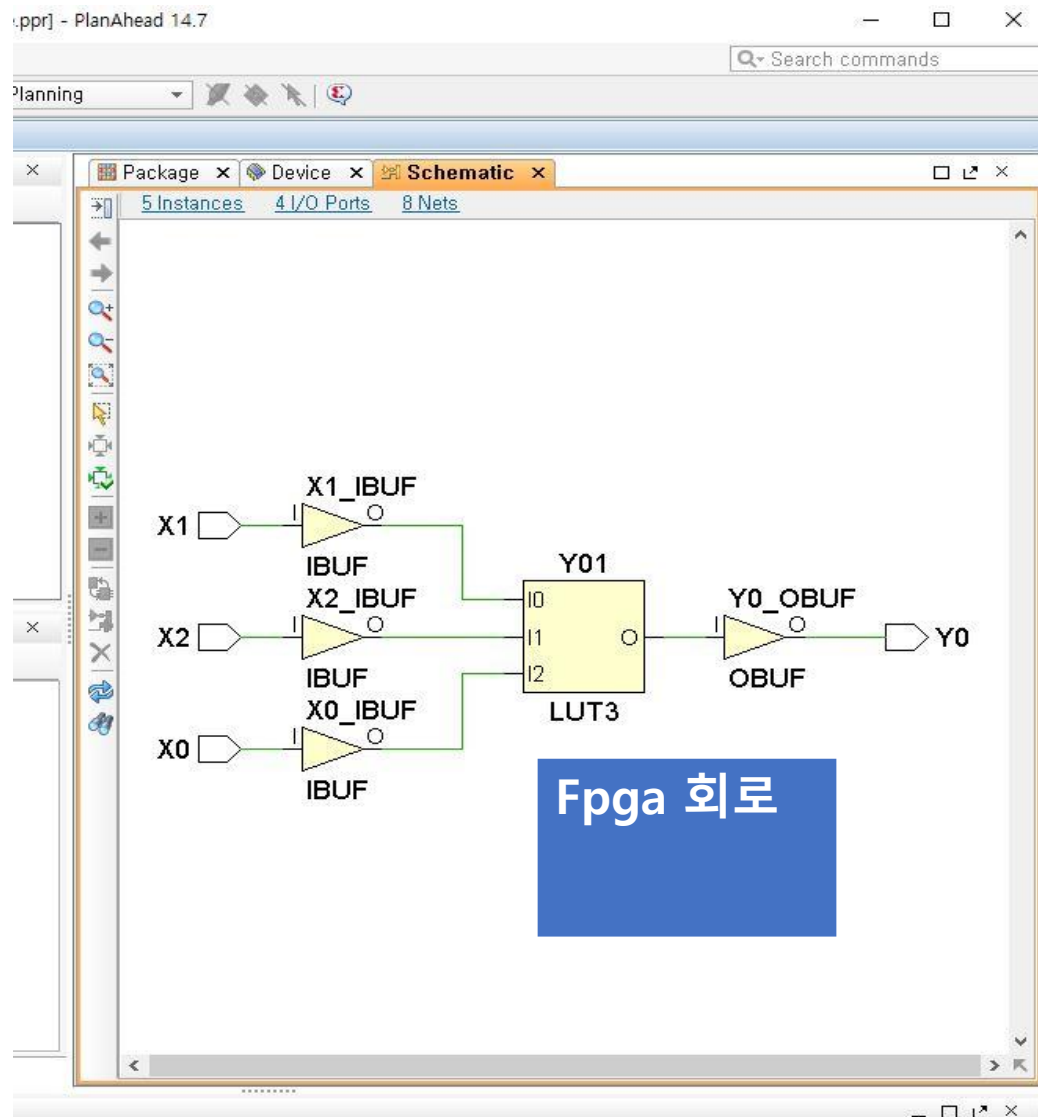

실습3 OR게이트 (시뮬레이션 화면)


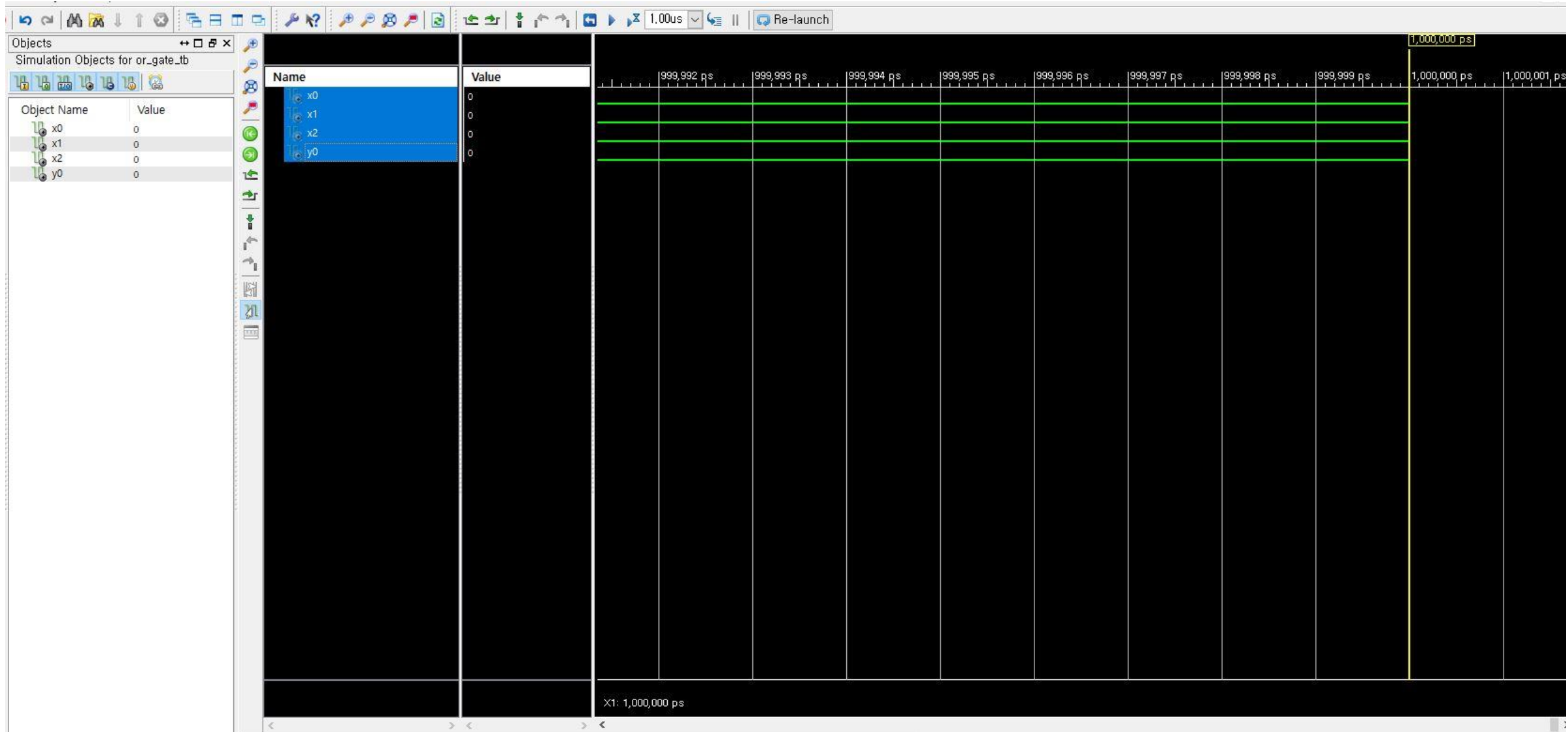


과제 All Gate 동작테이블

1입력 출력 동작 Table		2입력 출력 동작 Table			
X0 (스위치)	Y0 (LED)	X0 (스위치)	X1 (스위치)	Y1 (LED) OR 게이트	Y2 (LED) XOR 게이트
0	1	0	0	0	0
1	0	0	1	1	1
		1	0	1	1
		1	1	1	0

3입력 출력 동작 Table (X0, X1 우선입력)					
X0 (스위치)	X1 (스위치)	X2 (스위치)	Y3(LED) NAND게이트	Y4(LED) NOR게이트	Y5(LED) XNOR게이트
0	0	0	1	0	0
1	0	0	1	1	1
0	1	0	1	1	1
0	0	1	0	0	1
1	1	0	1	1	0
0	1	1	0	0	0
1	0	1	0	0	0
1	1	1	1	0	1

과제 All Gate (가상회로, fpqa 회로)

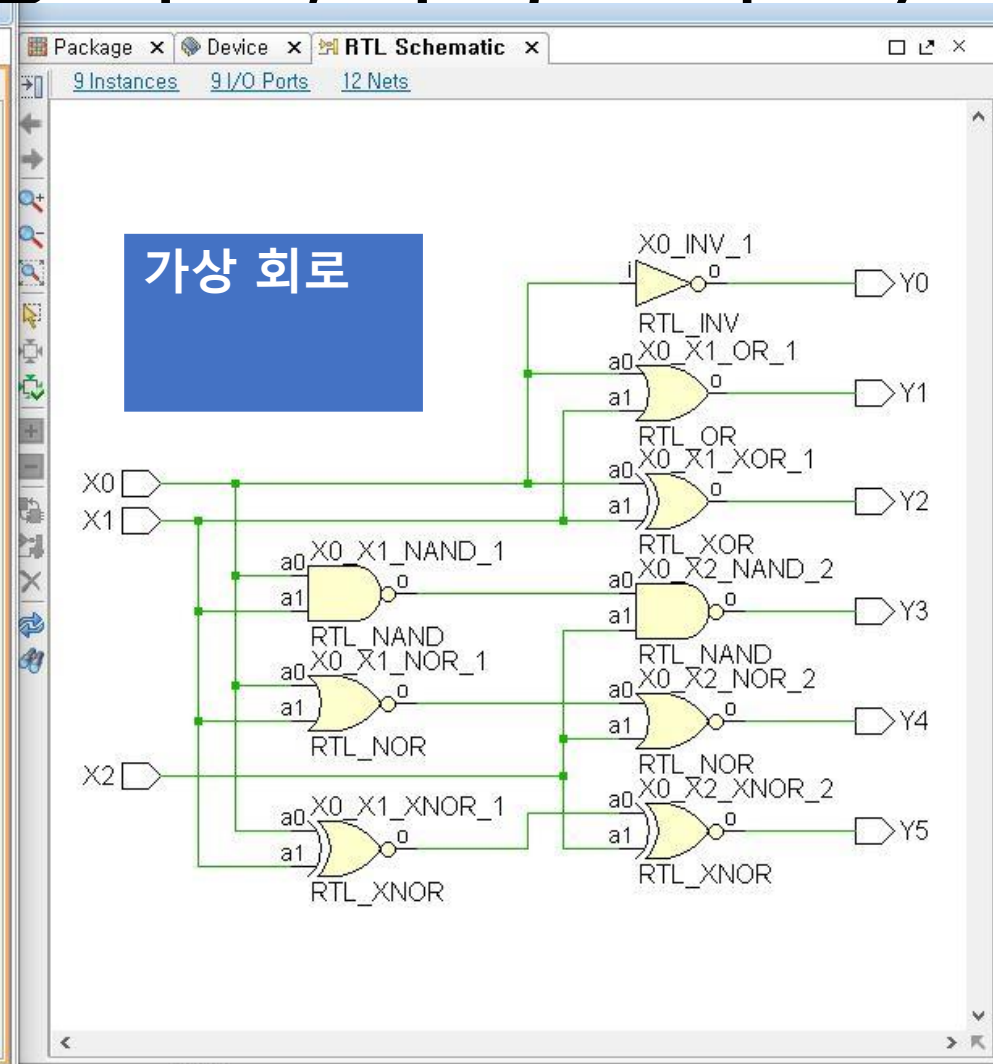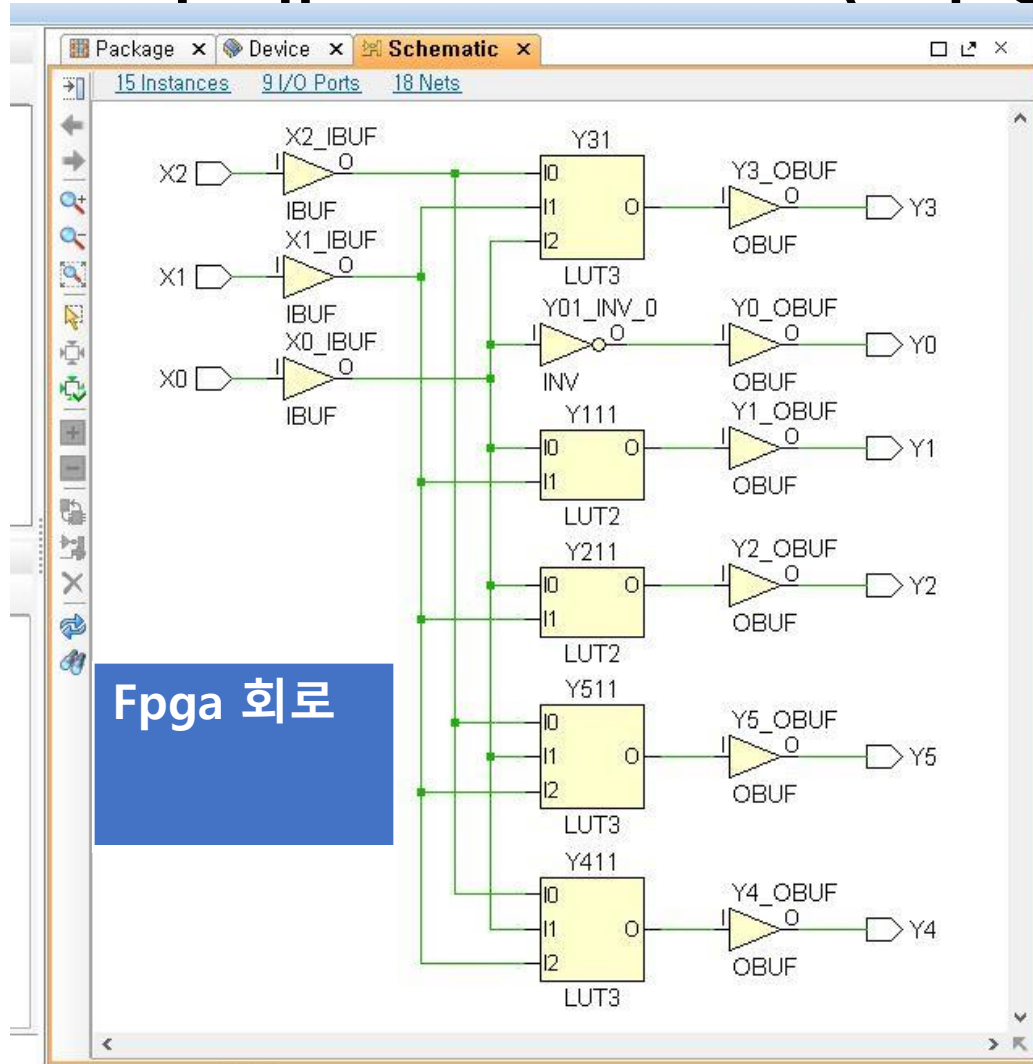

Pair	Site	Fixed	Bank	I/O Std	Vcco	Vref	Drive Str...	Slew
------	------	-------	------	---------	------	------	--------------	------

Site	Fixed	Bank	I/O Std	Vcco	Vref	Drive Str...	Slew
------	-------	------	---------	------	------	--------------	------

과제 All Gate (시뮬레이션 화면)

