

week11 과제

2학년_2반_2021041089_최태민

과제 : 동작테이블



X2 = 0, X1 = 0 일 때				
X3	X0	X2	X1	Y0
0	0	0	0	X
0	1	0	0	X
1	0	0	0	X
1	1	0	0	X

X2 = 0, X1 = 1 일 때				
X3	X0	X2	X1	Y0
0	0	0	1	1
0	1	0	1	0
1	0	0	1	1
1	1	0	1	0

X2 = 1, X1 = 0 일 때				
X3	X0	X2	X1	Y0
0	0	1	0	1
0	1	1	0	1
1	0	1	0	0
1	1	1	0	0

X2 = 1, X1 = 1 일 때				
X3	X0	X2	X1	Y0
0	0	1	1	1
0	1	1	1	1
1	0	1	1	0
1	1	1	1	0

과제 : 가상회로, fpga 회로

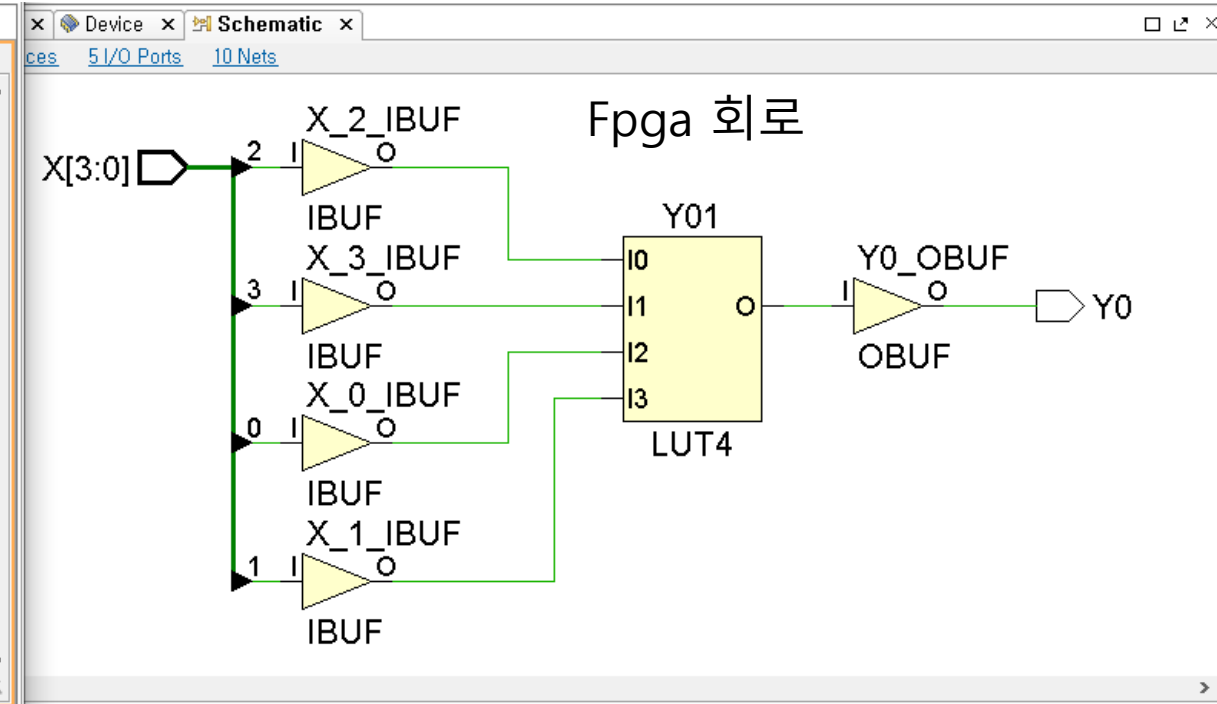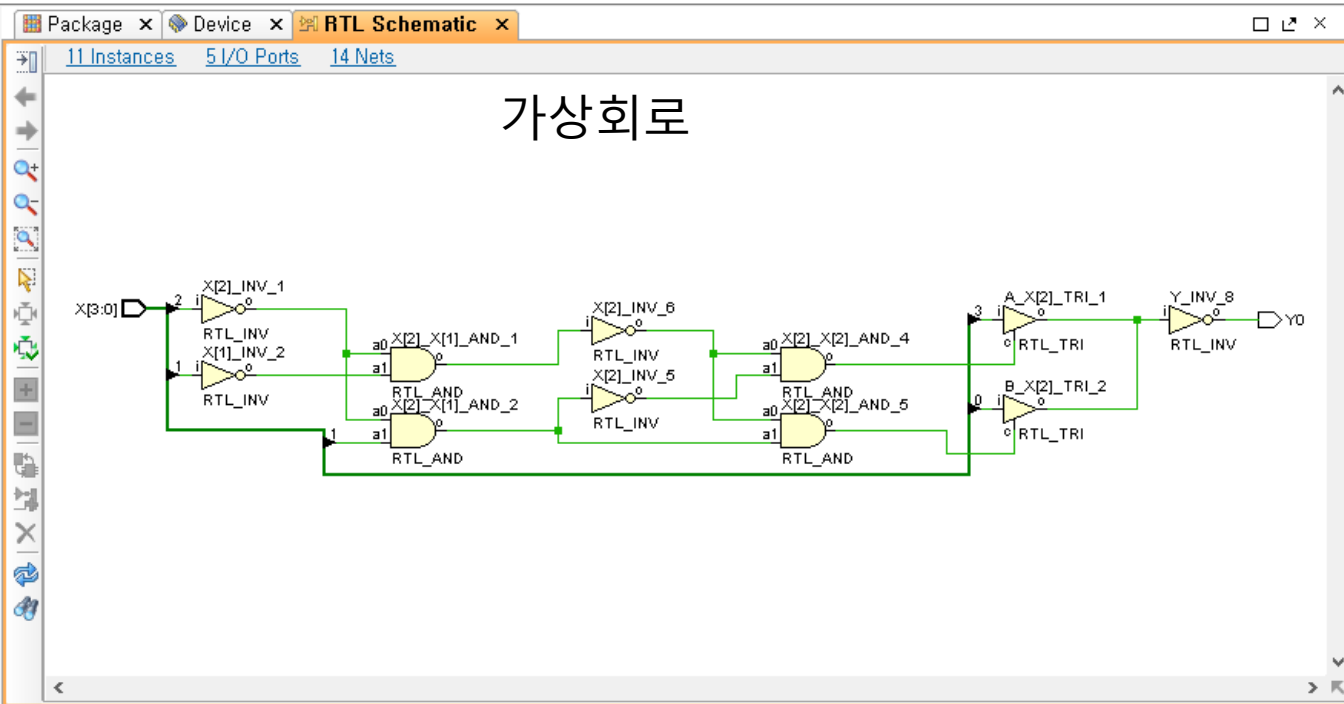

과제 : 시뮬레이션화면

